

Dr. Waheed Ahmad Younis

Do not submit this homework. There will be a quiz from this homework on Wednesday (Sep 30, 2021).

**Topics covered in this week:**

- First order filters

LPF:  $G(s) = \frac{\omega_0}{s + \omega_0}$     HPF:  $G(s) = \frac{s}{s + \omega_0}$     Where  $\omega_0 = \frac{R}{L}$  or  $\frac{1}{RC}$     Pole location:  $s = -\omega_0$   
Roll off = 20 dB/decade

- Second order filters

LPF:  $G(s) = \frac{\omega_0^2}{s^2 + (\omega_0/Q)s + \omega_0^2}$     Where  $\omega_0 = \frac{1}{\sqrt{LC}}$     and     $Q = R\sqrt{\frac{C}{L}}$  or  $\frac{1}{R}\sqrt{\frac{L}{C}}$


$G(j\omega) = \frac{\omega_0^2}{\omega_0^2 - \omega^2 + j\omega(\omega_0/Q)} = \frac{1}{1 - (\omega/\omega_0)^2 + j(\omega/\omega_0)Q}$

$|G(j\omega)| = \frac{1}{\sqrt{\{1 - (\omega/\omega_0)^2\}^2 + (\omega/\omega_0)Q^2}}$


$20 \log |G(j\omega)| = -10 \log[\{1 - (\omega/\omega_0)^2\}^2 + (\omega/\omega_0)Q^2] = \begin{cases} 0 \text{ dB} & \text{if } \omega \ll \omega_0 \\ -40 \log \frac{\omega}{\omega_0} \text{ dB} & \text{if } \omega \gg \omega_0 \end{cases}$

$20 \log |G(j\omega)| = 20 \log Q$     if  $\omega = \omega_0$


Roll off = 40 dB/decade

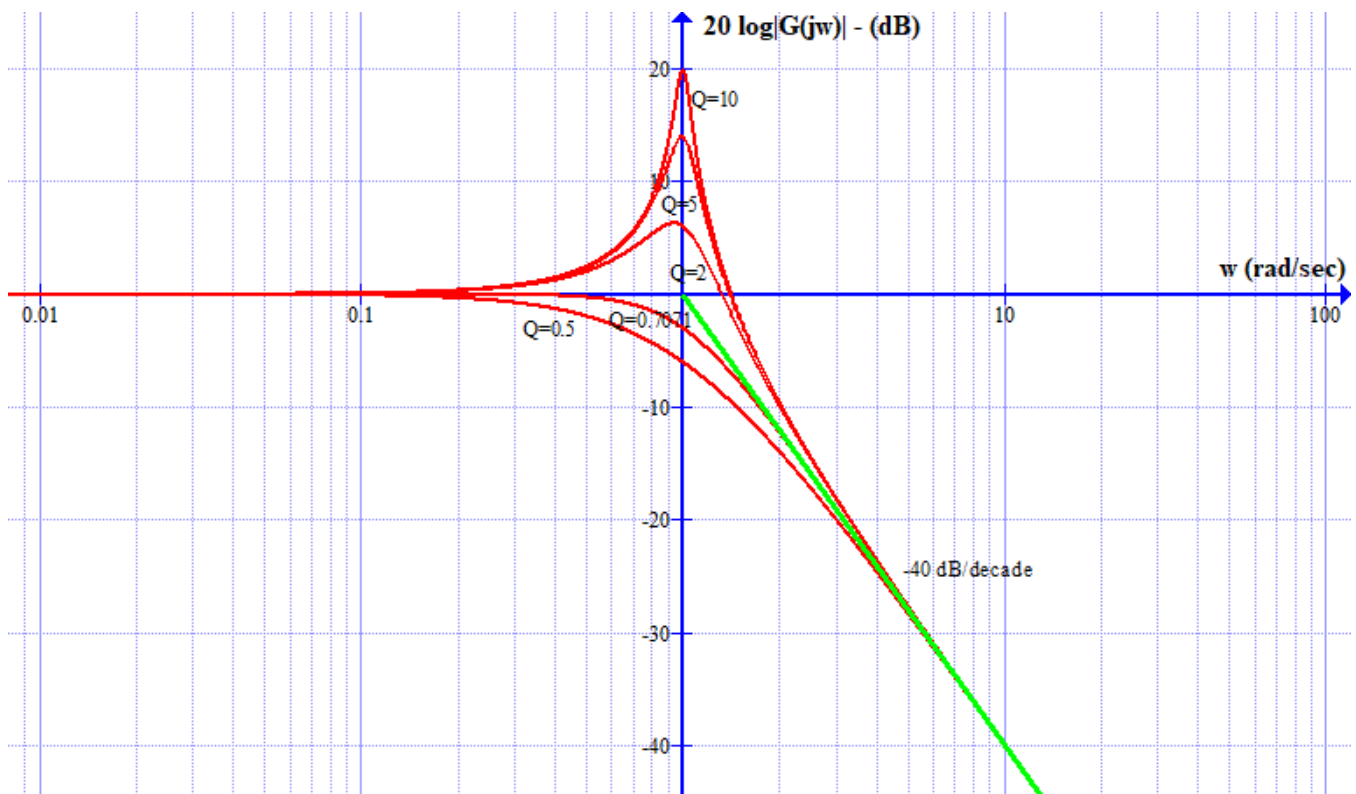

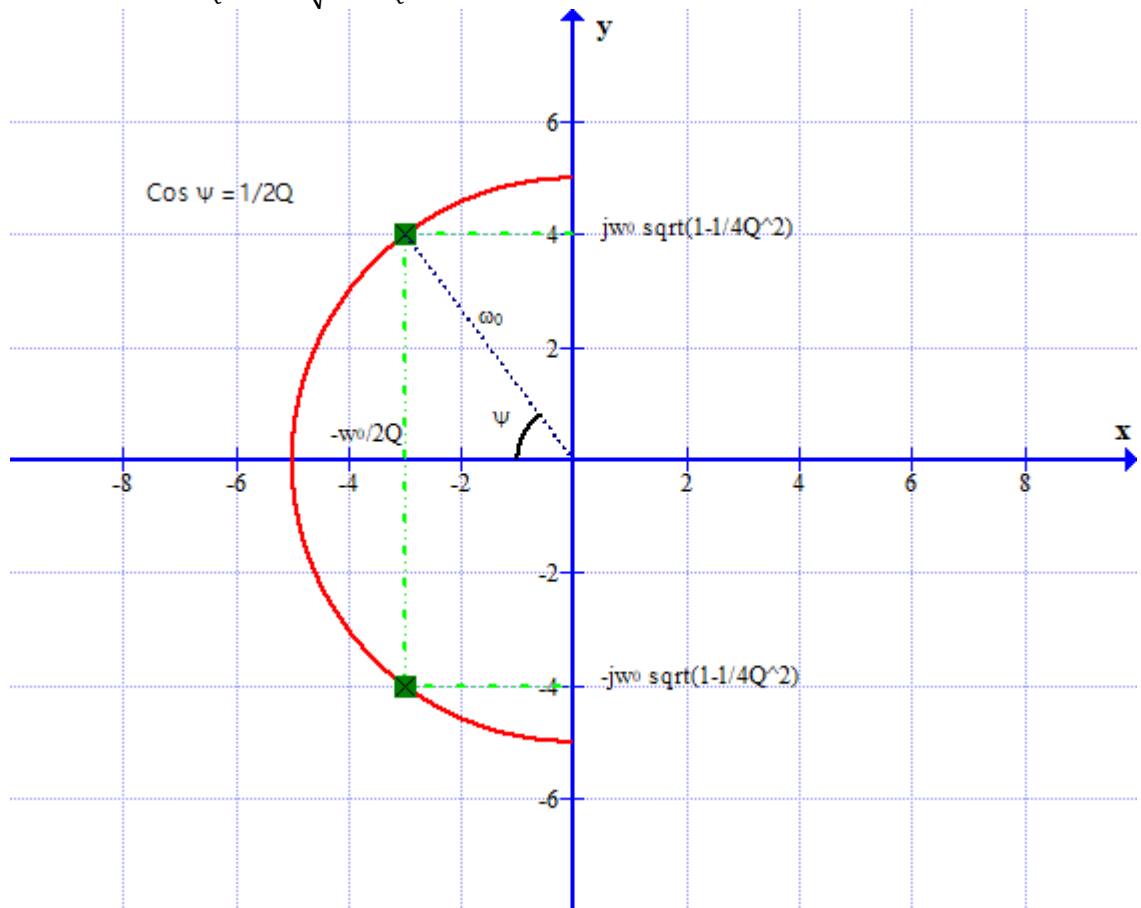Pole location:  $s_1, s_2 = -\frac{\omega_0}{2Q} \pm j\omega_0 \sqrt{1 - \frac{1}{4Q^2}}$



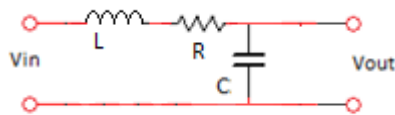**Q1.** Consider the following passive LPF:



If  $C=0.05\mu\text{F}$ ,  $L=16\text{mH}$  and  $R=120\Omega$

- Drive the transfer function.
- Find the poles and zeros of the filter.
- Calculate  $\omega_0$  and  $Q$ . What is the peak gain and at which frequency is it observed?
- Redesign the circuit to raise its  $Q$  to 12 without changing  $\omega_0$ .
- Confirm your answers by plotting the frequency responses of the original and redesigned circuits.

**Solution:**

a. Transfer function:  $G(s) = \frac{1/LC}{s^2 + (R/L)s + 1/LC} = \frac{\omega_0^2}{s^2 + (\omega_0/Q)s + \omega_0^2}$

Where  $\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(16 \times 10^{-3})(0.05 \times 10^{-6})}} = 35,355 \text{ rad/s}$

$Q = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{120} \sqrt{\frac{16 \times 10^{-3}}{0.05 \times 10^{-6}}} = 4.714$

b. Poles:  $s_1, s_2 = -\frac{\omega_0}{2Q} \pm j\omega_0 \sqrt{1 - \frac{1}{4Q^2}} = -\frac{35,355}{2(4.714)} \pm j35,355 \sqrt{1 - \frac{1}{4(4.714)^2}} = -3,750 \pm j35,156$


c.  $\omega_0 = 35,355 \text{ rad/s}$   
 $Q = 4.714$

$$\text{Peak gain} = Q \sqrt{1 - \frac{1}{4Q^4}} = 4.714 \sqrt{1 - \frac{1}{4(4.714)^2}} = 4.713$$


$$\text{Frequency of peak gain} = \omega_0 \sqrt{1 - \frac{1}{2Q^2}} = 34,955 \text{ rad/s}$$

d. Q will be 12 if:  $R = \frac{1}{Q} \sqrt{\frac{L}{C}} = \frac{1}{12} \sqrt{\frac{16 \times 10^{-3}}{0.05 \times 10^{-6}}} = 47.14 \Omega$

e.

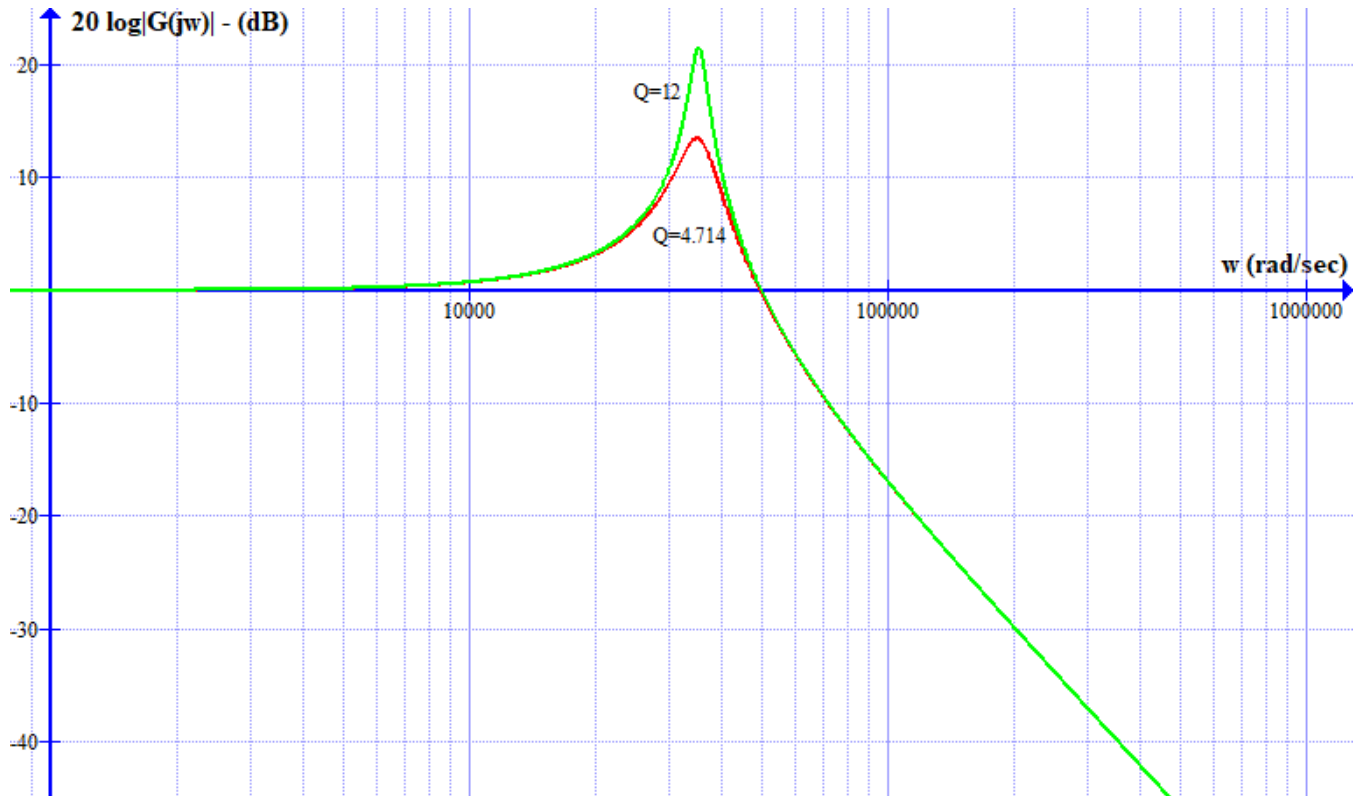

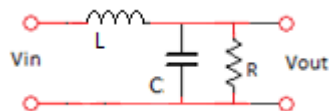**Q2.** Consider the following passive LPF circuit:



It is required that the poles should be located at  $s_1, s_2 = 1,000e^{\pm j\frac{3\pi}{4}}$

- Calculate  $\omega_0$  and  $Q$ .
- Find the values of  $R$ ,  $L$  &  $C$ .

**Solution:**

a.  $\omega_0 = 1,000 \text{ rad/s}$        $Q = \frac{1}{2 \cos \psi} = \frac{1}{2 \cos 45^\circ} = \frac{1}{\sqrt{2}} = 0.7071$

b.  $\omega_0 = \frac{1}{\sqrt{LC}} = 1,000$     and     $Q = R \sqrt{\frac{C}{L}} \Rightarrow \sqrt{\frac{C}{L}} = \frac{Q}{R} = \frac{0.7071}{R}$

Let  $R = 70.71 \Omega$

$$\sqrt{\frac{C}{L}} = \frac{Q}{R} = \frac{0.7071}{70.71} = \frac{1}{100}$$

$$\frac{1}{\sqrt{LC}} \sqrt{\frac{C}{L}} = (1,000) \left( \frac{1}{100} \right) \Rightarrow L = 0.1 \text{ H}$$

$$C = 10^{-4}(L) = 10^{-4}(0.1) = 100 \mu\text{F}$$