


Dr. Waheed Ahmad Younis

Do not submit this homework. There will be a quiz from this homework on Thursday (Oct 07, 2021).

Topics covered in this week:


Second order passive filters

- LPF:

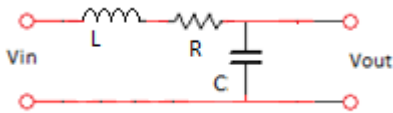

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

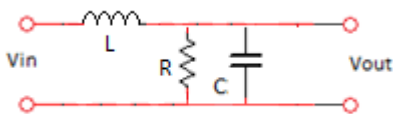


$$Q = R \sqrt{\frac{C}{L}}$$


$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$G(s) = \frac{\omega_0^2}{s^2 + (\omega_0/Q)s + \omega_0^2}$$

$$20 \log|G(j\omega)| = -10 \log[1 - (\omega/\omega_0)^2]^2 + (\omega/\omega_0 Q)^2] = \begin{cases} 0 \text{ dB} & \text{if } \omega \ll \omega_0 \\ -40 \log \frac{\omega}{\omega_0} \text{ dB} & \text{if } \omega \gg \omega_0 \\ 20 \log Q \text{ dB} & \text{if } \omega = \omega_0 \end{cases}$$

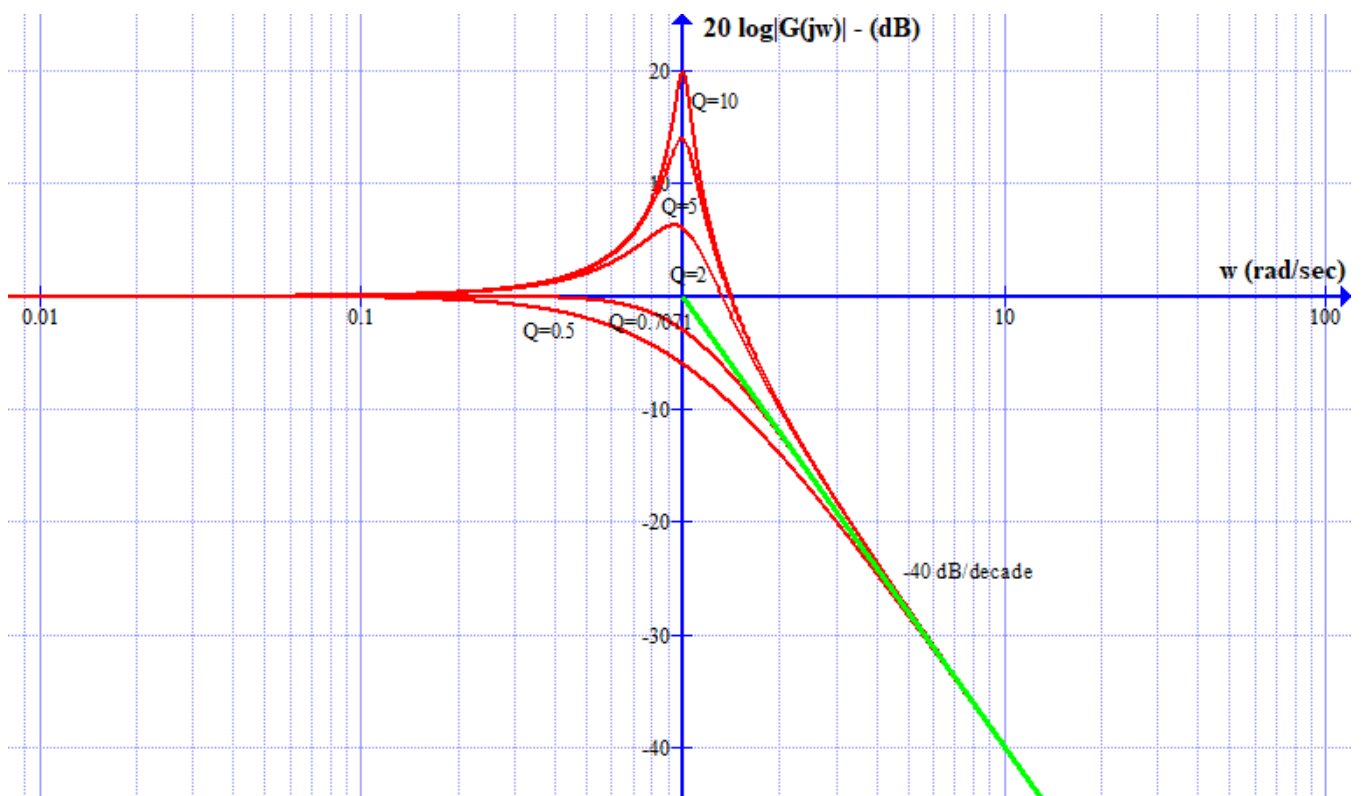


- HPF:

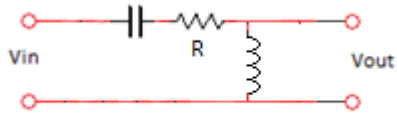

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

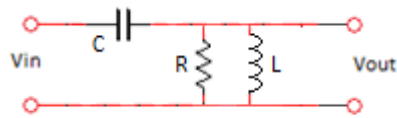


$$Q = R \sqrt{\frac{C}{L}}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$


$$G(s) = \frac{s^2}{s^2 + (\omega_0/Q)s + \omega_0^2}$$

$$20 \log|G(j\omega)| = 40 \log(\omega/\omega_0) - 10 \log[1 - (\omega/\omega_0)^2]^2 + (\omega/\omega_0 Q)^2] =$$
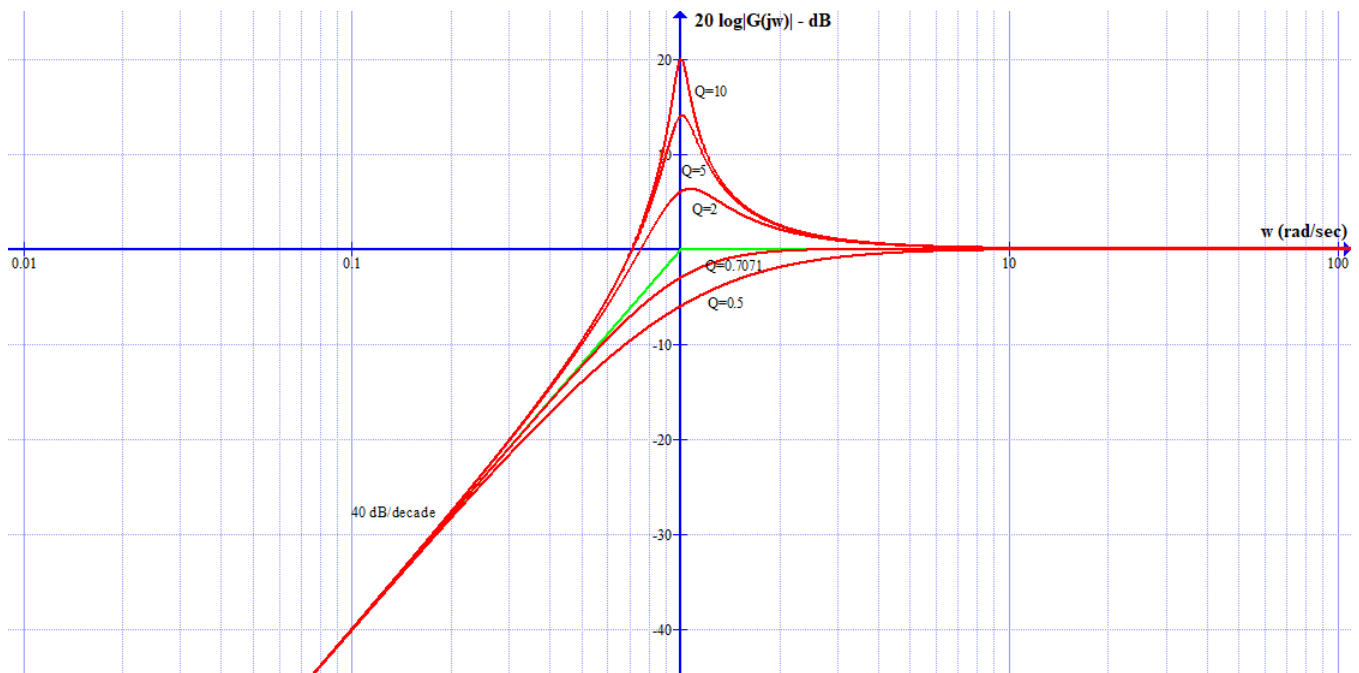
$$\begin{cases} 40 \log \frac{\omega}{\omega_0} \text{ dB} & \text{if } \omega \ll \omega_0 \\ 0 \text{ dB} & \text{if } \omega \gg \omega_0 \\ 20 \log Q \text{ dB} & \text{if } \omega = \omega_0 \end{cases}$$




- BPF:

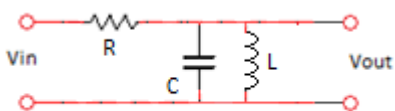

$$Q = R \sqrt{\frac{C}{L}}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

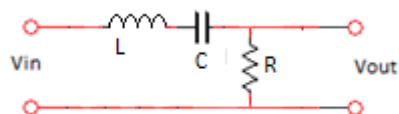


$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$G(s) = \frac{(\omega_0/Q)s}{s^2 + (\omega_0/Q)s + \omega_0^2}$$

$$20 \log|G(j\omega)| = 20 \log(\omega/\omega_0 Q) - 10 \log[1 - (\omega/\omega_0)^2]^2 + (\omega/\omega_0 Q)^2] =$$
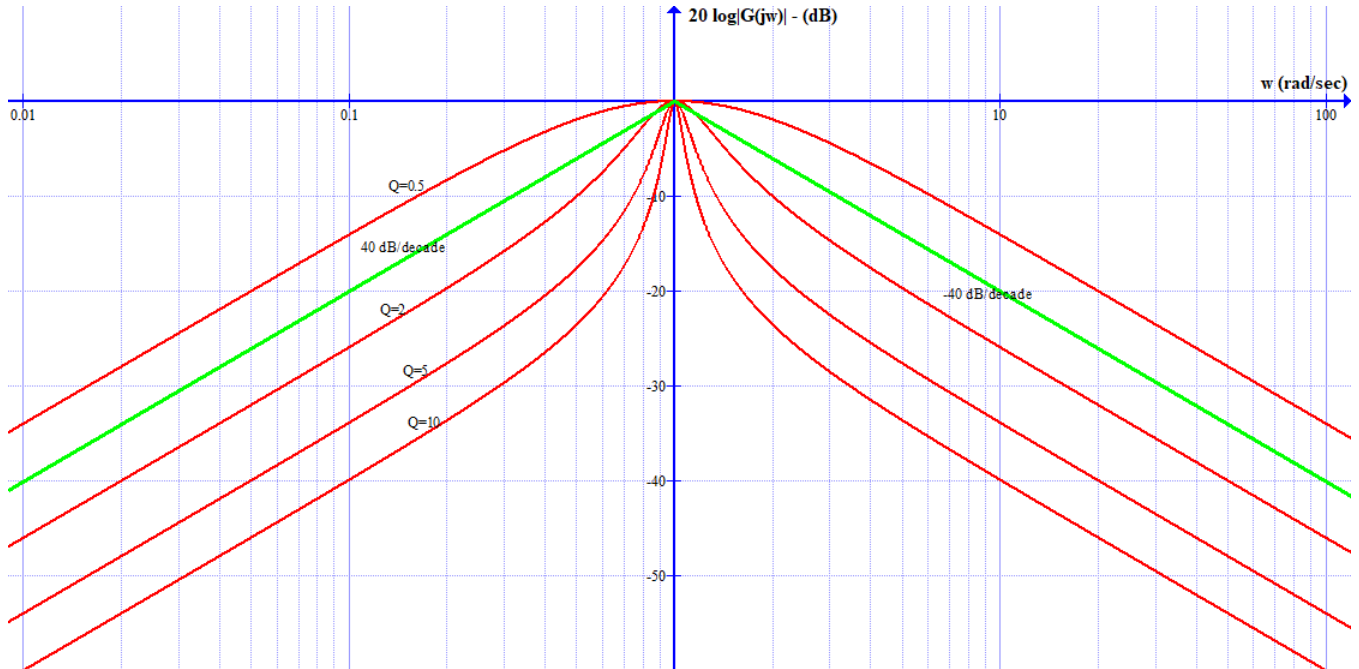
$$\begin{cases} 20 \log(\omega/\omega_0 Q) & \text{if } \omega \ll \omega_0 \\ -20 \log(\omega Q/\omega_0) & \text{if } \omega \gg \omega_0 \\ 0 \text{ dB} & \text{if } \omega = \omega_0 \end{cases}$$




$$\text{Upper cut-off frequency: } \omega_u = \omega_0 \sqrt{1 + \frac{1}{4Q^2}} + \frac{\omega_0}{2Q}$$

$$\text{Lower cut-off frequency: } \omega_l = \omega_0 \sqrt{1 + \frac{1}{4Q^2}} - \frac{\omega_0}{2Q}$$

$$\text{Bandwidth: } BW = \omega_u - \omega_l = \frac{\omega_0}{Q} \Rightarrow Q = \frac{\omega_0}{BW}$$

$$\text{Also: } \omega_0 = \sqrt{\omega_u \omega_l}$$

- BRF:

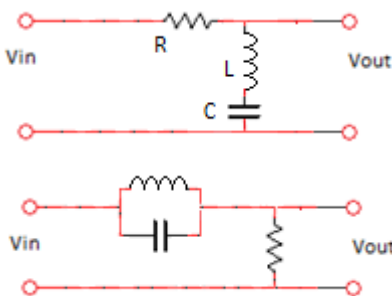

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$Q = R \sqrt{\frac{C}{L}}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$G(s) = \frac{s^2 + \omega_0^2}{s^2 + (\omega_0/Q)s + \omega_0^2}$$

$$20 \log|G(j\omega)| = 20 \log \left[1 - \left(\frac{\omega}{\omega_0} \right)^2 \right]^2 - 10 \log \left[1 - \left(\frac{\omega}{\omega_0} \right)^2 \right]^2 + \left(\frac{\omega}{\omega_0 Q} \right)^2 \right] = \begin{cases} 0 \text{ dB} & \text{if } \omega \ll \omega_0 \\ 0 \text{ dB} & \text{if } \omega \gg \omega_0 \\ -\infty \text{ dB} & \text{if } \omega = \omega_0 \end{cases}$$



$$G_{LP}(s) = \frac{\omega_0^2}{s^2 + (\omega_0/Q)s + \omega_0^2}$$

$$G_{HP}(s) = \frac{s^2}{s^2 + (\omega_0/Q)s + \omega_0^2}$$

$$G_{BP}(s) = \frac{(\omega_0/Q)s}{s^2 + (\omega_0/Q)s + \omega_0^2}$$

$$G_{BR}(s) = \frac{s^2 + \omega_0^2}{s^2 + (\omega_0/Q)s + \omega_0^2}$$