

Dr. Waheed Ahmad Younis

Do not submit this homework. There will be a quiz from this homework on Thursday (Oct 14, 2021).

Topics covered in this week:

Active filters

- First order:



- LPF

Gain of the non-inverting amplifier = $K = 1 + \frac{R_y}{R_x}$

Transfer function: $G(s) = \frac{K\omega_0}{s+\omega_0}$ where $\omega_0 = \frac{1}{RC}$

- HPF

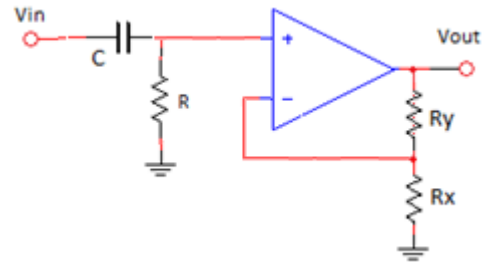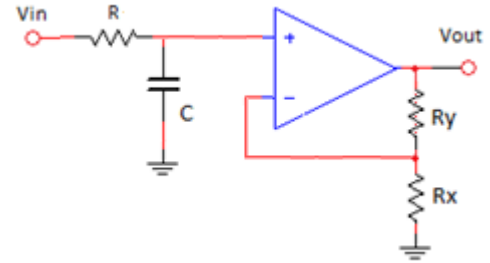Transfer function: $G(s) = \frac{Ks}{s+\omega_0}$ where $\omega_0 = \frac{1}{RC}$



- Sallen-Key circuit (2nd order filter)


$$G(s) = \frac{K/R_1R_2C_1C_2}{s^2 + \left(\frac{1}{R_1C_1} + \frac{1}{R_2C_2} + \frac{1}{R_2C_1} - \frac{K}{R_2C_2}\right)s + 1/R_1R_2C_1C_2}$$

Where $K = 1 + \frac{R_y}{R_x}$

Replacing $\omega_0^2 = \frac{1}{R_1R_2C_1C_2}$

and $\frac{1}{Q} = \sqrt{\frac{R_2C_2}{R_1C_1}} + \sqrt{\frac{R_1C_2}{R_2C_1}} + \sqrt{\frac{R_1C_1}{R_2C_2}}(1 - K)$
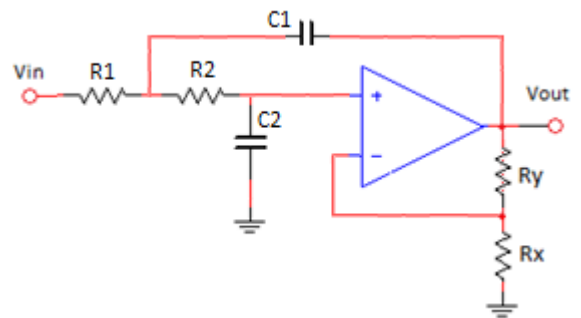
$$G(s) = \frac{K\omega_0^2}{s^2 + \left(\frac{\omega_0}{Q}\right)s + \omega_0^2}$$



- Butterworth (maximally flat) LP filter

Q1. Design a 1st order LP filter with a gain of 5 at zero frequency. Cut-off frequency is 1 kHz.

Solution:

Transfer function of the active LP first order filter: $G(s) = \frac{K\omega_0}{s+\omega_0}$

$$G(j\omega) = \frac{K\omega_0}{j\omega + \omega_0} = \frac{K}{1 + j\omega/\omega_0} \quad |G(j\omega)| = \frac{K}{\sqrt{1 + (\omega/\omega_0)^2}} \quad |G(j0)| = K$$

$K = 1 + \frac{R_y}{R_x} = 5$ $R_y = 4R_x$ If $R_x = 2 \text{ k}\Omega$ then $R_y = 8 \text{ k}\Omega$

$\frac{1}{RC} = 2\pi(10^3)$ if $C = 0.1 \mu\text{F}$, $R = \frac{1}{2,000\pi(0.1 \times 10^{-6})} = 1592 \Omega = 1.59 \text{ k}\Omega$

Q2. Design a 2nd order LP filter with Q=0.7071 and cut-off frequency 1 kHz. Gain is not specified.

Solution:

For Sallen-Key circuit, if $R_1 = R_2 = R$ and $C_1 = C_2 = C$, then $\omega_0 = \frac{1}{RC}$ and $Q = \frac{1}{3-K}$

If $Q=0.7071$, $K=3-1/Q=3-1/0.7071=1.586$

$K = 1 + \frac{R_y}{R_x} = 1.586$ $R_y = 0.586R_x$ If $R_x = 10 \text{ k}\Omega$ then $R_y = 5.86 \text{ k}\Omega$

$C = 0.1 \mu\text{F}$, and $R = 1.59 \text{ k}\Omega$ will give $f_0 = 1 \text{ kHz}$

Q3. Design a 2nd order LP filter with $Q=0.7071$ and cut-off frequency 1 kHz. Gain is unity at zero frequency.

Solution:

For Sallen-Key circuit, if $K=1$, $\frac{1}{Q} = \sqrt{\frac{R_2 C_2}{R_1 C_1}} + \sqrt{\frac{R_1 C_2}{R_2 C_1}}$. Now assuming $R_1 = R_2 = R$, $Q = \frac{1}{2} \sqrt{\frac{C_1}{C_2}}$, $C_1 = 2C_2$

If $C_2 = 0.1 \mu\text{F}$, $C_1 = 0.2 \mu\text{F}$

$\omega_0^2 = \frac{1}{R^2 C_1 C_2}$ $\omega_0 = \frac{1}{R \sqrt{C_1 C_2}}$ $R = \frac{1}{2,000\pi \sqrt{(0.1 \times 10^{-6})(0.2 \times 10^{-6})}} = 1125 \Omega = 1.125 \text{ k}\Omega$

$K=1$ if $R_y = 0$ and $R_x = \infty$.

Q4. Design a 5th order Butterworth LP filter with cut-off frequency 1 kHz.

Solution:

For 5th order filter, the poles are located on unit circle at: $0^\circ, \pm 36^\circ, \pm 72^\circ$. Pole locations would be $s_1 = -1$, $s_2, s_3 = -\cos 36 \pm j \sin 36$, $s_4, s_5 = -\cos 72 \pm j \sin 72$ [note that the critical frequency is normalized to 1 rad/s]

The denominator would be

$(s+1)(s^2+2\cos 36+1)(s^2+2\cos 72+1) = (s+1)(s^2+1.618s+1)(s^2+0.618s+1)$

We can make the 5th order filter by cascading 3 filters:

$\left(\frac{1}{s+1}\right) \left(\frac{1}{s^2+1.618s+1}\right) \left(\frac{1}{s^2+0.618s+1}\right)$

For all the filters, $K=1$.

For 1st filter (1st order): $C = 0.1 \mu\text{F}$, and $R = 1.59 \text{ k}\Omega$

For 2nd filter (2nd order): $Q=1/1.618=0.618$ $R_1 = R_2 = R$ $Q = \frac{1}{2} \sqrt{\frac{C_1}{C_2}} = 0.618$ $C_1 = 1.53C_2$

If $C_2 = 0.1 \mu\text{F}$, $C_1 = 0.153 \mu\text{F}$

$\omega_0^2 = \frac{1}{R^2 C_1 C_2}$ $\omega_0 = \frac{1}{R \sqrt{C_1 C_2}}$ $R = \frac{1}{2,000\pi \sqrt{(0.1 \times 10^{-6})(0.153 \times 10^{-6})}} = 1287 \Omega = 1.287 \text{ k}\Omega$

$K=1$ if $R_y = 0$ and $R_x = \infty$.

For 3rd filter (2nd order): $Q=1/0.618=1.618$ $R_1 = R_2 = R$ $Q = \frac{1}{2} \sqrt{\frac{C_1}{C_2}} = 1.618$ $C_1 = 10.47C_2$

If $C_2 = 0.1 \mu\text{F}$, $C_1 = 1.047 \mu\text{F}$

$\omega_0^2 = \frac{1}{R^2 C_1 C_2}$ $\omega_0 = \frac{1}{R \sqrt{C_1 C_2}}$ $R = \frac{1}{2,000\pi \sqrt{(0.1 \times 10^{-6})(1.047 \times 10^{-6})}} = 492 \Omega$

$K=1$ if $R_y = 0$ and $R_x = \infty$.

