

Dr. Waheed Ahmad Younis

Do not submit this homework. There will be a quiz from this homework on Thursday (Oct 21, 2021).

Topics covered in this week:

- Butterworth (maximally flat) LP filter design
 - Identifying the pole location
 - Forming the proper denominator polynomial (1st and 2nd order expressions)
 - Designing the filter using op-amps and resistors, capacitors

- Magnitude function of Butterworth filter of order n

$$|G(j\omega)| = \frac{1}{\sqrt{1+(\omega/\omega_0)^{2n}}} \quad 20 \log|G(j\omega)| = G_{dB} = -10 \log[1 + (\omega/\omega_0)^{2n}]$$

- Filter design based on given specifications

Given: ω_p , ω_s , G_{min} and G_{max} find ω_0 and n

$$\omega_0 = \frac{\omega}{[10^{-G_{dB}/10} - 1]^{1/2n}} \quad \text{and} \quad n = \frac{\log \left[\frac{(10^{-G_{min}/10} - 1)}{(10^{-G_{max}/10} - 1)} \right]}{2 \log(\omega_p/\omega_s)}$$

- Filter designing using frequency scaling and impedance scaling.
 - Design the filter for a normalized frequency of 1 rad/s
 - Frequency scale by dividing L and C by ω_0 .
 - Impedance scale by multiplying R and L by some factor Z and divide C by same factor Z.
 - Design of Butterworth HP filter
 - Design the corresponding LP filter first
 - Interchange Rs and Cs with appropriate values
 - Properly scale (frequency scale and impedance scale) to get the real circuit
-

Q1. You have to design a Butterworth LP filter. Passband should be up to 2.5 kHz. Stopband should be above 3.5 kHz. In the passband, filter gain should not be below -0.4 dB and in stopband, the filter gain should not be more than -30 dB. Find the order of the required filter and a proper choice of ω_0 .

Solution:

Given:

$$\omega_p = 2\pi(2,500) \text{ rad/s}$$

$$\omega_s = 2\pi(3,500) \text{ rad/s}$$

$$G_{min} = -0.4 \text{ dB}$$

$$G_{max} = -30 \text{ dB}$$

$$n = \frac{\log \left[\frac{(10^{-G_{min}/10} - 1)}{(10^{-G_{max}/10} - 1)} \right]}{2 \log(\omega_p/\omega_s)} = \frac{\log \left[\frac{(10^{0.4/10} - 1)}{(10^{30/10} - 1)} \right]}{2 \log(2.5/3.5)} = 13.74 \quad \text{So, } n = 14.$$


Using ω_p :

$$f_0 = \frac{f}{[10^{-G_{dB}/10} - 1]^{1/2n}} = \frac{f_p}{[10^{-G_{min}/10} - 1]^{1/2n}} = \frac{2,500}{[10^{0.4/10} - 1]^{1/28}} = 2.718 \text{ kHz}$$

Using ω_s :

$$f_0 = \frac{f}{[10^{-G_{dB}/10} - 1]^{1/2n}} = \frac{f_s}{[10^{-G_{max}/10} - 1]^{1/2n}} = \frac{3,500}{[10^{30/10} - 1]^{1/28}} = 2.735 \text{ kHz}$$

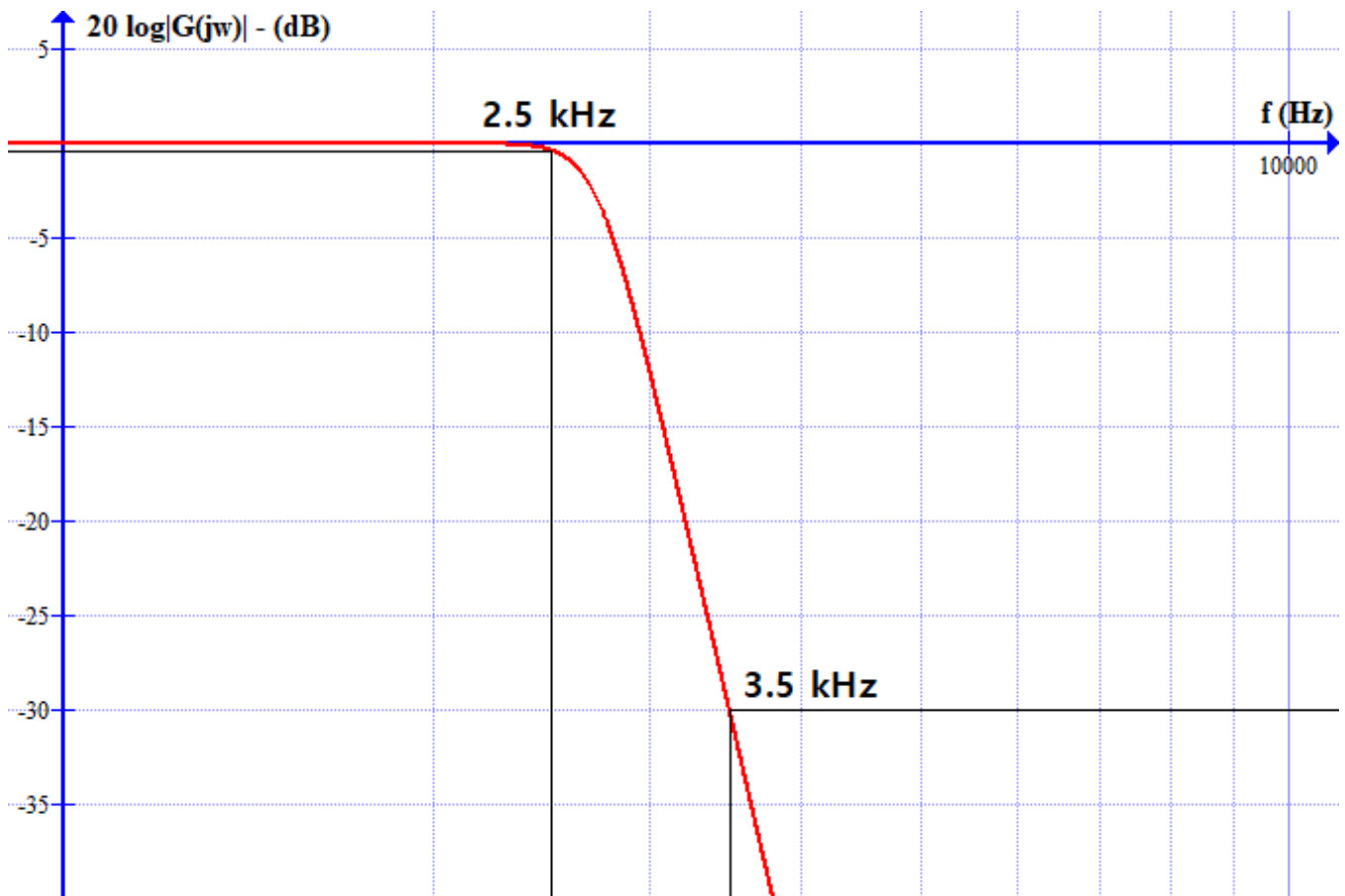We recommend using: $f_0 = 2.726 \text{ kHz}$




Q2. Consider a normalized Sallen-Key circuit with the following component values:

$$R_1 = R_2 = 1 \Omega$$

$$C_1 = 2Q F, \quad C_2 = \frac{1}{2Q} F$$

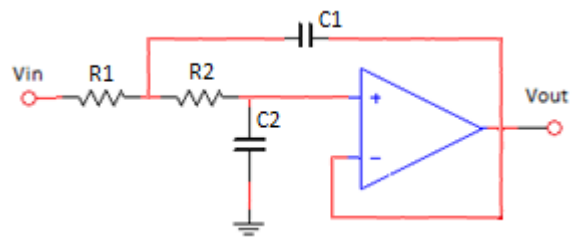Perform proper scaling and design a 2nd order LP filter with $Q = 1.2$ and cut-off frequency 2.3 kHz.



Solution:

Initial (normalized values):

$$R_1 = R_2 = 1 \Omega$$

$$C_1 = 2.4 F, \quad C_2 = 0.4167 F$$

After frequency scaling:

$$R_1 = R_2 = 1 \Omega$$

$$C_1 = 166 \mu F, \quad C_2 = 28.832 \mu F$$

After impedance scaling:

$$R_1 = R_2 = 1 k\Omega$$


$$C_1 = 0.166 \mu F, \quad C_2 = 0.0288 \mu F$$

Q3. Design a 2nd order HP filter with Q = 0.8 and cut-off frequency 1.3 kHz.

Solution:

Consider the LP Sallen-Key circuit normalized to $\omega_0 = 1$.

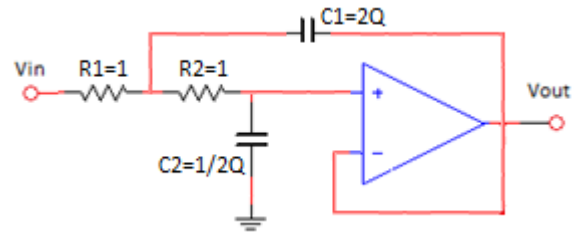Transfer function for this circuit is $G(s) = \frac{1}{s^2 + \frac{s}{Q} + 1}$



Interchanging Cs and Rs, we get the circuit for HP filter with transfer function

$$G(s) = \frac{s^2}{s^2 + \frac{s}{Q} + 1}$$

Let us calculate the component values for this HP filter:

Initial (normalized values):

$$C_1 = C_2 = 1 \text{ F}$$

$$R_1 = 0.625 \Omega, \quad R_2 = 1.6 \Omega$$

After frequency scaling:

$$C_1 = C_2 = 122.43 \mu\text{F}$$

$$R_1 = 0.625 \Omega, \quad R_2 = 1.6 \Omega$$

After impedance scaling:

$$C_1 = C_2 = 0.122 \mu\text{F}$$

$$R_1 = 625 \Omega, \quad R_2 = 1.6 \text{ k}\Omega$$

